

Supervision 12
Jiachen Jiang

Read the following sections of the handouts:

Section 6

Problem Sheet – Q18 - Q24

Q22

Remove “The cable to the probe contributes an additional capacitance of 45pF between the oscilloscope input and the ground.” in the question. Instead, use the circuit diagram below for this question.

